

Module -2


Single Phase AC Circuits -

The resistance, inductance & capacitance are the three basic elements of any elect. ckt. In order to analyse any elect. ckt, it is necessary to understand

- 1) AC through pure resistive ckt
- 2) ————— inductive ckt
- 3) ————— capacitive ckt

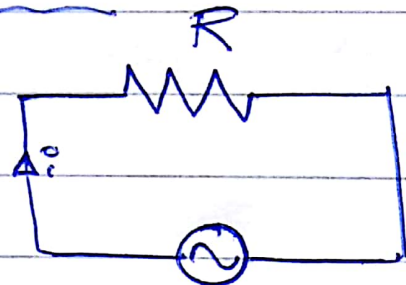1. AC through pure Resistive Circuit -

Consider a pure resistive ckt with a resistance of R ohms connected across a sinusoidal v_g v . given by



$$v = V_m \sin \omega t \quad \text{--- (1)}$$

$$v = V_m \sin \omega t$$

By ohms law, instantaneous i in the ckt is

$$i = \frac{v}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t$$

$$= I_m \sin \omega t. \quad \text{--- (2)}$$

where $I_m = V_m / R$.

Comparing eq^s (1) & (2), it is clear that v_g & i are in phase with each other. i.e phase diff. betⁿ them is zero.

Power

$$\text{Inst. power } p = v \times i.$$

$$= V_m \sin \omega t \times I_m \sin \omega t$$

$$= V_m I_m \sin^2 \omega t$$

$$= V_m I_m \frac{(1 - \cos 2\omega t)}{2}$$


$$= \frac{V_m I_m}{2} - \frac{V_m I_m \cos 2\omega t}{2}$$

For a one complete cycle, the avg value of $\frac{V_m I_m \cos 2\omega t}{2}$ is zero.

$$\therefore \text{Avg power for whole cycle } P = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}}$$


$$= VI \text{ Watts.}$$

where V & I are RMS values of v & i.

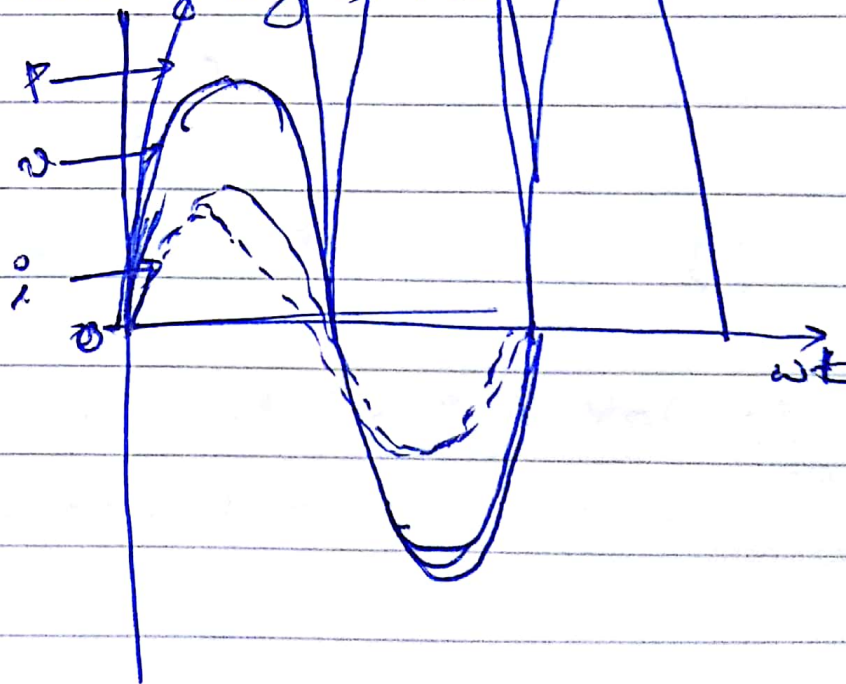

AC through a purely Inductive Circuit —

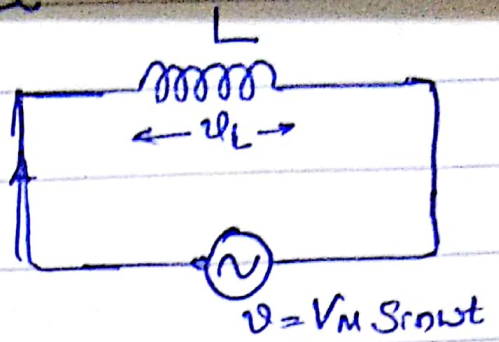C₂, an ac ckt consisting of a pure inductance of L Henry. Let the inst. value of applied v_g is $v = V_m \sin \omega t$ — (1)



This ac v_g will cause an ac c_t 'i' to flow through the ckt. Due to the inductance of the coil, a self induced emf is induced in the coil, which opposes the applied v_g at every instant.

$$\therefore v_L = -L \frac{di}{dt}$$

By applying KVL

$$v - v_L = 0 \quad \text{or} \quad V_m \sin \omega t = L \frac{di}{dt}$$

$$\therefore \frac{di}{dt} = \frac{V_m}{L} \sin \omega t$$

Integrating both sides,

$$\int \frac{di}{dt} = \int \frac{V_m}{L} \sin \omega t$$

$$\Rightarrow i = \frac{V_m}{L} \left(-\frac{\cos \omega t}{\omega} \right)$$

$$= \frac{V_m}{\omega L} (-\cos \omega t) = \frac{V_m}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

C_t is max. when $\sin \left(\omega t - \frac{\pi}{2} \right) = 1 \quad \therefore I_m = \frac{V_m}{\omega L} = \frac{V_m}{X_L}$

where X_L is inductive reactance = ωL measured in Ohms


$$\therefore i = I_m \sin \left(\omega t - \frac{\pi}{2} \right) \quad \text{--- (2)}$$

Comparing eq^s ① & ⑤ ~~we get~~ it is clear that ct always lags the applied vg by an angle 90° or $\frac{\pi}{2}$ rad.

Power

$$\begin{aligned}\text{Instantaneous power } p &= v i \\ &= V_m \sin \omega t \cdot I_m \sin (\omega t - \frac{\pi}{2}) \\ &= -V_m I_m \sin \omega t \cdot \cos \omega t \\ &= -\frac{V_m I_m}{2} \sin 2\omega t.\end{aligned}$$

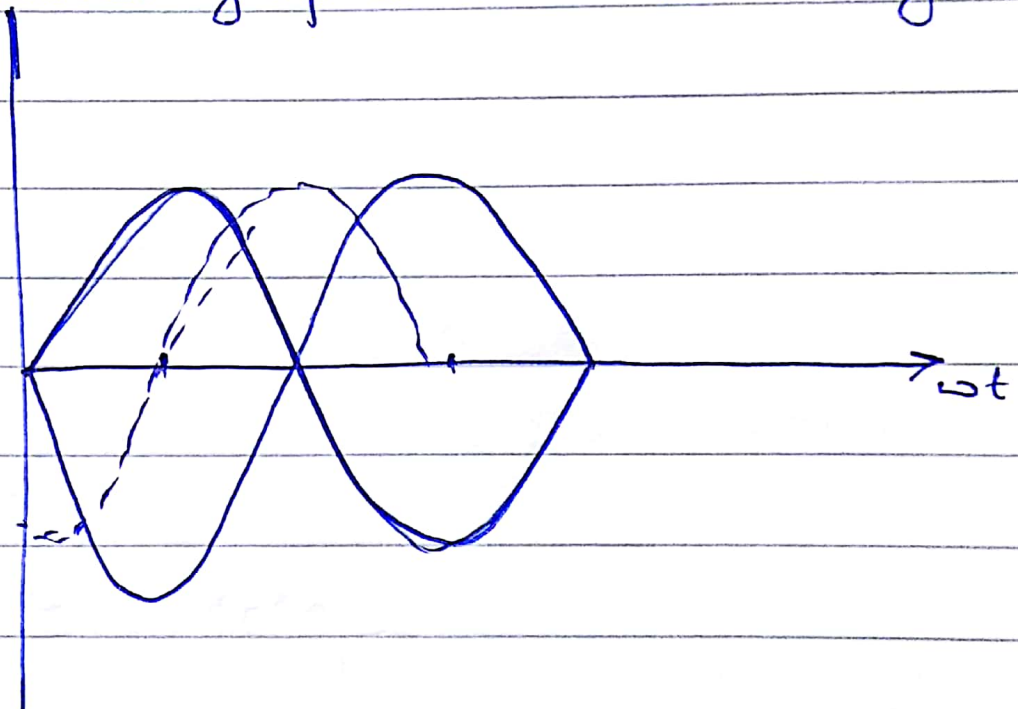
The avg power consumed by a pure inductive ckt over a cycle is zero.



$$\begin{aligned}P &= \frac{1}{2\pi} \int_0^{2\pi} -\frac{V_m I_m}{2} \sin 2\omega t \\ &= -\frac{V_m I_m}{4\pi} \left(-\frac{\cos 2\omega t}{2} \right) \Big|_0^{2\pi} \\ &= 0\end{aligned}$$

AC through pure Capacitive Ckt.:

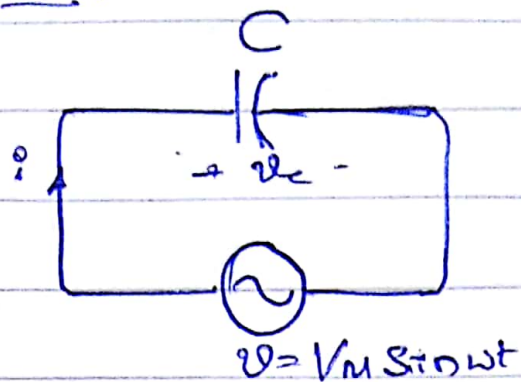Let $v = V_m \sin \omega t$ be the applied vg. a/c a capacitor of capacitance C Farads



Inst. charge $q = Cv = C V_m \sin \omega t$

Capacitor ct is equal to the rate of change of charge

$$\Rightarrow i = \frac{dq}{dt} = \frac{d}{dt} C V_m \sin \omega t$$

$$= \omega C V_m \cos \omega t$$

$$= \frac{V_m}{1/\omega C} \cos \omega t$$

CIVIL

$$= \frac{V_m}{X_c} \cos \omega t = I_m \sin (\omega t + \pi/2)$$

$$X_c = 1/\omega C = 1/2\pi f C$$

In pure capacitive ckt ct leads vg. by $\pi/2$ or 90°

Power

$$p = v \times i$$

$$= \frac{V_m I_m}{2} \cos 2\omega t$$

Avg power over a full cycle is zero.

$P = 0$ Hence, power consumed by a pure capacitance in a ac ckt is zero.


AC through R-L Circuit

$$\vec{V} = \vec{V}_R + \vec{V}_L$$

$$\vec{V} = \vec{IR} + \vec{IX}_L$$

$$\vec{IR} = \vec{IR} + \vec{IX}_L$$

$$\Rightarrow \vec{Z} = R + jX_L$$

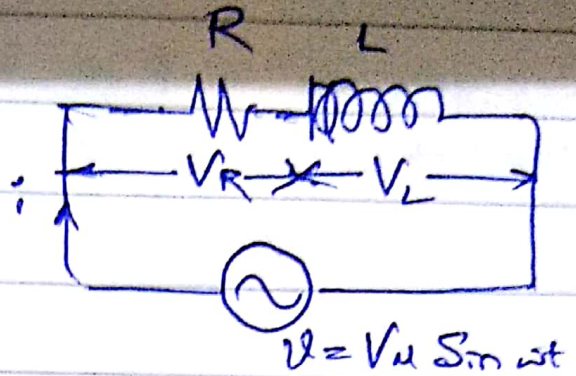


From vector diagram

$$V = \sqrt{V_R^2 + V_L^2}$$

$$\Rightarrow Z = \sqrt{R^2 + X_L^2}$$

$$\& i = I_m \sin(\omega t - \phi)$$

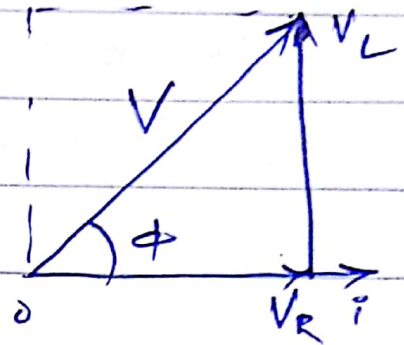


Power — $P = V_R I = V \cos \phi I = VI \cos \phi$

$$\vec{V} = \vec{V}_R + \vec{V}_L$$

$$\vec{VI} = \vec{V}_R I + \vec{V}_L I$$

$$= VI \cos \phi + VI \sin \phi$$

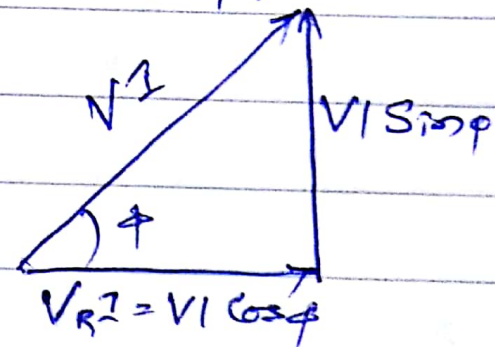

These three terms are defined as

(1) Apparent Power (S)

It is the product of rms values of v (V) & i (A)

& is denoted by $S = V \times I$. VA

It is measured in volt-amp (VA) or kilo-volt-amp (KVA)

DATE

(2) Real or True or Active Power (P):

It is the product of applied vg & active component of the ct. It is measured in watts (W) or kilo watts (kW)

$$P = VI \cos \phi \text{ watts}$$

(3) Reactive Power (Q):

It is the product of applied vg & reactive component of the ct. Its unit is Volt-ampere-reactive (VAR).

$$Q = VI \sin \phi \text{ VAR}$$

Power Factor:

It is defined as a factor by which the apparent power must be multiplied in order to obtain true power.

It is the ratio of ^{true} ~~apparent~~ power to ^{apparent} ~~true~~ power

$$\text{Power Factor} = \frac{\text{True Power}}{\text{Apparent Power}} = \frac{VI \cos \phi}{VI} = \cos \phi$$

It is the cosine of the angle between applied vg & ct drawn from the supply. It cannot be greater than 1.

It is also defined as ratio of resistance to impedance

$$\cos \phi = R/Z$$

The nature of p.f is always determined by position of ct w.r. to vg leading or lagging.

Ex: A 100V, 50 Hz inductive ckt takes a ct of 10A lagging the vg by 30° . Calculate the resistance & inductance of the ckt.

Given: $V = 100V$, $f = 50Hz$, $I = 10A$, $\phi = 30^\circ$

$$\therefore I = 10 \angle -30^\circ \text{ A.}$$

$$\begin{aligned} \therefore Z &= \frac{V}{I} = \frac{100 \angle 0^\circ}{10 \angle -30^\circ} = 10 \angle 30^\circ \Omega \\ &= 8.66 + j5 \Omega \end{aligned}$$

$$\therefore R = 8.66 \Omega \quad \& \quad X_L = 5 \Omega$$

$$2\pi fL = 5 \Omega \quad \therefore L = 0.0159 \text{ H.}$$

Ex: A series R-L ckt takes 400W at a p.f of 0.8 across a 120V, 50Hz supply. Calculate the values of R & L.

Sol: Given: $P = 400W$, $f = 50Hz$, $V = 120V$, $\cos \phi = 0.8$

$$P = VI \cos \phi$$

$$400 = 120 \times I \times 0.8 \quad \text{or } I = 4.167 \text{ A}$$

$$\therefore Z = V/I = 28.8 \Omega$$

$$\text{WKT } \cos \phi = R/Z \quad \text{or } R = Z \cos \phi = 23.04 \Omega$$

$$\& \quad \tan \phi = X_L/R \quad \text{or } X_L = R \tan \phi = 17.27 \Omega$$

$$X_L = 2\pi fL = 17.27 \Omega$$

$$\therefore L = 0.055 \Omega$$

Ex: An emf of $v = 220 \sin(314t - 1.5708) \text{ V}$ is applied to a series ckt. The ct flowing is $i = 20 \sin(314t - 10^\circ) \text{ A}$. Find the freq. & the values of ckt elements.

Solⁿ: $v = 220 \sin(314t - 1.5708) \text{ V}$

$$\therefore V_m = 220 \text{ V} \quad \& \quad \phi = -1.5708 \text{ rad} = -90^\circ$$

$$\omega = 314 \quad \therefore f = 50 \text{ Hz}$$

$$i = 20 \sin(314t - 10^\circ)$$

$$\therefore I_m = 20 \text{ A} \quad \& \quad \phi = -10^\circ$$

$$V = \frac{V_m}{\sqrt{2}} = 155.56 \text{ V} \quad \& \quad I = \frac{I_m}{\sqrt{2}} = 14.142 \text{ A}$$

$$\therefore V = 155.56 \angle -90^\circ \text{ V} \quad \& \quad I = 14.142 \angle -10^\circ \text{ A}$$

$$\therefore Z = \frac{V}{I} = 11 \angle -80^\circ \Omega$$

$$= 1.91 - j10.832 \Omega$$

$$\therefore R = 1.91 \Omega \quad \& \quad X_C = 10.832 \Omega$$

$$\therefore C = 2.93 \times 10^{-4} \text{ F}$$

Exⁿ

Ex: An alternating vg of $(160 + j120) \text{ V}$ is applied to a ckt. & the ct is given by $(6 + j8) \text{ A}$. Find the values of ckt elements ~~as for~~ 50 Hz freq. Also calculate power factor of the ckt & power consumed.

Ex: A certain v_g is applied to a series R-L-C ckt. The v_g a/c these elements are 170V, 150V. & 100V resp. The ct drawn is 4A. Find the p.f. of the ckt.

Solⁿ

$$V_R = IR$$

$$\text{OR } R = 42.5 \Omega$$


$$V_L = IX_L$$

$$\therefore X_L = 37.5 \Omega \quad V_C = IX_C \quad \therefore X_C = 25 \Omega$$

$$\therefore Z = \sqrt{R^2 + (X_L - X_C)^2} = 44.3 \Omega$$

$$\cos \phi = R/Z = 0.9593, \text{ Lag.}$$

Lagging because $X_L > X_C$

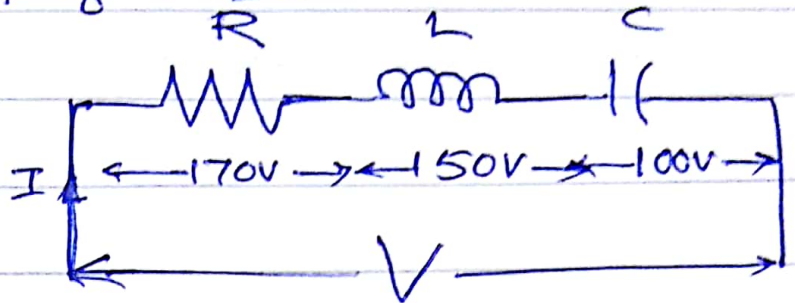

Ex: A series RLC ckt has $R = 100 \Omega$, $L = 0.1 \text{ H}$ & $C = 5 \mu\text{F}$

A v_g $v(t) = 141.4 \cos 377t \text{ V}$ is applied to the ckt

Det. the ~~avg~~ ct, & v_g s of V_R , V_L & V_C .

Solⁿ: $v(t) = 141.4 \cos 377t$

$$\text{OR } = 141.4 \sin(377t + 90^\circ)$$


$$\therefore V_m = 141.4, \omega = 377$$

$$\therefore V = V_m / \sqrt{2} = 100 \text{ V}$$

$$V = 100 \angle 90^\circ \text{ V} \quad X_L = \omega L = 377 \angle 90^\circ \Omega \quad X_C = 530.5 \angle -90^\circ \Omega$$

$$Z_T = R + X_L + X_C = 183.20 \angle -56.917^\circ \Omega$$
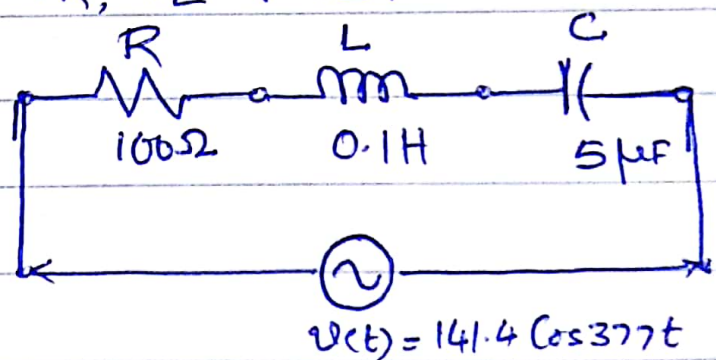
$$I = V/Z_T = 0.5458 \angle 146.917^\circ \text{ A}$$



$$\therefore V_R = I \times R = 54.58 \text{ } \underline{146.917} \text{ V}$$

$$V_L = I \times X_L = 205.766 \text{ } \underline{236.917} \text{ V}$$

$$V_C = I \times X_C = 289.549 \text{ } \underline{56.917} \text{ V}$$

$$\therefore |V_R| = 54.58 \text{ V}, \quad |V_L| = 205.766 \text{ V} \quad |V_C| = 289.549 \text{ V}$$